

# EC39004 – VLSI Laboratory Verilog Module

Name : Rekha Lokesh

Roll No : 19EC10052


Group : 3

## Expt 4: Basic Processor Structural

### Objective:

- Write a Structural Verilog code to synthesize the given Basic Processor Operations.
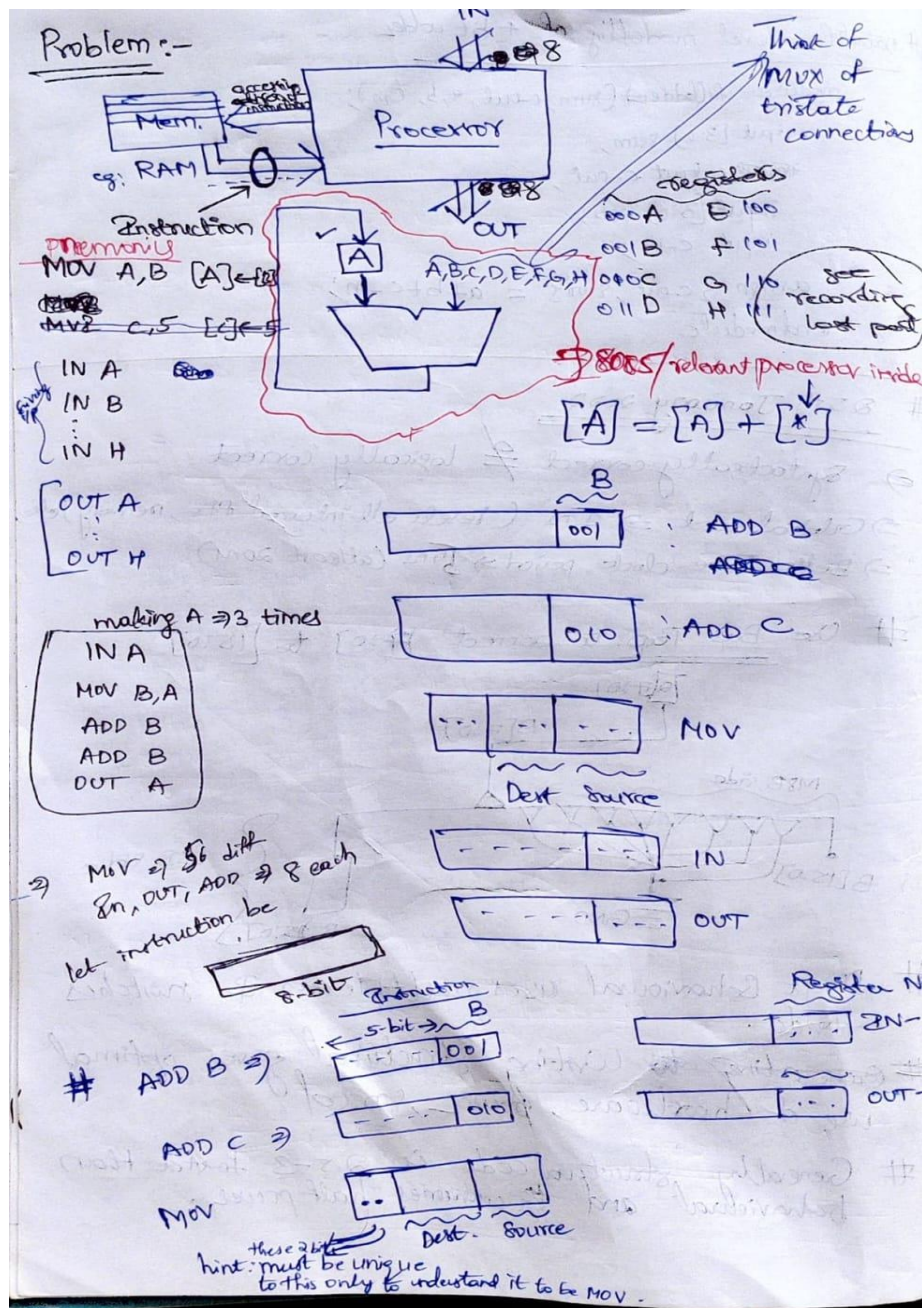
### Class Discussion and Problem Statement



# Think processor has only 3 ports  
IN, OUT and Instruction ports:

4 operations of Processor

ADD  
MOV  
IN  
OUT

first two bits are sufficient to detect in 8 bit instruction

eg: Using these instructions, make

IN A  
MOV BA  
ADD A  
ADD B  
OUT A


//  $B \leftarrow A$

//  $A \leftarrow A + A$  i.e.,  $A \leftarrow 2A$

//  $A \leftarrow A + B \Rightarrow A$  becomes thrice of initial value

⇒ Give Hardware to user to write codes like this

#

 

Whether they become X (don't care) or how are they used?

In up versions, we use these 3 bits to change manually of A

i.e.,  $C \leftarrow A + B$  or  $A \leftarrow D + E$  instead of  $A \leftarrow A + X$


### Design approach/steps:

- The instruction, load, clock and Reset are 4 input ports and 'out' is an output port to the system.
- Instruction is 8 bits wide** where the **two most significant bits are used as select lines** to multiplex for the operation and **the next three bits are for destination register** and **next three for source register**.



- The 8 storage registers are defined as **A, B, C,..., H** and their 3 bit binary values are **000, 001,...,111** respectively.
- The operations according to instr[7:6] are:
  - 00 -> Input Load into REGN (source register) -> LD REGN
  - 01 -> Move REGP to REGN -> MOV REGN REGP
  - 10 -> Add A to REGP and Store in REGN -> ADD REGN REGP
  - 11 -> Output REGP (destination register) -> OUT REGP
- The ADDER is designed using a macro and the rest individual components like 8:1 MUX, 4:1 MUX, 2:1 MUX, 3to8 Decoder and Registers, individual modules are written in structural manner (without primitives) and all of them are **instantiated in the top module** according to the Circuit Followed below.
- As visible from the circuit, **4:1 MUX handles the operation, 8:1 MUX handles the source register, 3:8 Decoder handles the destination register** and the **AND gate is used to detect the OUT Case** where the Source Register is the Destination Register (handled by 2:1 MUX).
- After every given instruction, give **one cycle to the clock** so that any **edge triggered components** in the system move forward.
- For testcase, take the case of making the value of A thrice using the algorithm LD A -> MOV B A -> OUT B -> ADD A B -> ADD A B -> OUT A

## THE CIRCUIT DIAGRAM FOLLOWED

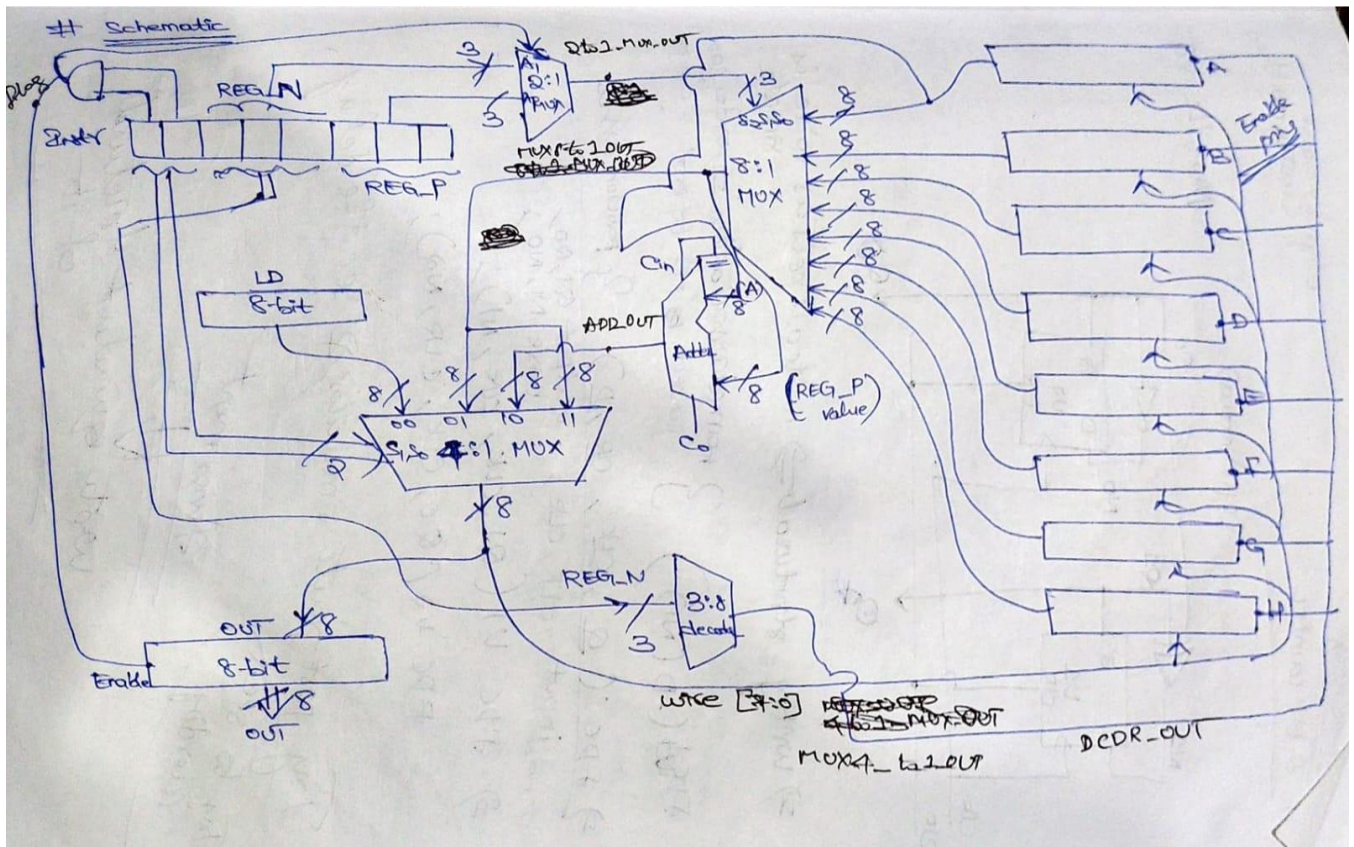

## Structural Verilog Code:

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 14:43:26 02/06/2022
// Design Name:
// Module Name: Basic_Processor_Struct
// Project Name:
// Target Devices:
// Tool versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////
module Basic_Processor_Struct(
    input [7:0] INSTR,
    input CLK, input RST,
    input [7:0] Load,
    output [7:0] OUT
);

    wire [2:0] MUX_2to1_OUT;
    wire [7:0] MUX_8to1_OUT, MUX_4to1_OUT, ADD_OUT, DCDR;
    wire [7:0] A_out, B_out, C_out, D_out, E_out, F_out, G_out, H_out;

    wire flag, Car_out;

    RGSTR8CE A(A_out, CLK, DCDR[0], RST, MUX_4to1_OUT);
    RGSTR8CE B(B_out, CLK, DCDR[1], RST, MUX_4to1_OUT);
    RGSTR8CE C(C_out, CLK, DCDR[2], RST, MUX_4to1_OUT);
    RGSTR8CE D(D_out, CLK, DCDR[3], RST, MUX_4to1_OUT);
    RGSTR8CE E(E_out, CLK, DCDR[4], RST, MUX_4to1_OUT);
    RGSTR8CE F(F_out, CLK, DCDR[5], RST, MUX_4to1_OUT);
    RGSTR8CE G(G_out, CLK, DCDR[6], RST, MUX_4to1_OUT);
    RGSTR8CE H(H_out, CLK, DCDR[7], RST, MUX_4to1_OUT);

    AND2 A1(flag, INSTR[7], INSTR[6]);
    MUX2_1 M1(MUX_2to1_OUT, INSTR[2:0], INSTR[5:3], flag);
    MUX8_1 M2(MUX_8to1_OUT, A_out, B_out, C_out, D_out, E_out, F_out, G_out, H_out, MUX_2to1_OUT);

    ADDSUB_MACRO #(
        .DEVICE("VIRTEX6"), // Target Device: "VIRTEX5", "VIRTEX6", "SPARTAN6"
        .LATENCY(0), // Desired clock cycle latency, 0-2
        .WIDTH(8) // Input / output bus width, 1-48
    ) ADDSUB_MACRO_inst (
        .CARRYOUT(Car_out), // 1-bit carry-out output signal
        .RESULT(ADD_OUT), // Add/sub result output, width defined by WIDTH parameter
        .A(MUX_8to1_OUT), // Input A bus, width defined by WIDTH parameter
        .ADD_SUB(1'b1), // 1-bit add/sub input, high selects add, low selects subtract
        .B(A_out), // Input B bus, width defined by WIDTH parameter
        .CARRYIN(1'b0), // 1-bit carry-in input
        .CE(1'b1), // 1-bit clock enable input
        .CLK(CLK), // 1-bit clock input
        .RST(RST) // 1-bit active high synchronous reset
    );

    MUX4_1 M3(MUX_4to1_OUT, Load, MUX_8to1_OUT, ADD_OUT, MUX_8to1_OUT, INSTR[7:6]);

    DCDR3_8 D1(DCDR, INSTR[5:3]);

    RGSTR8CE OTPT(OUT, CLK, flag, RST, MUX_4to1_OUT);

endmodule
```

```

module RGSTR8CE(output reg [7:0] OUT, input CLK, input CE, input CLR, input [7:0] D);
    always @(negedge CLK or posedge CLR)
        begin
            if(CLR)
                OUT = 8'd0;
            else
                if(CE)
                    begin
                        OUT = D;
                    end
                end
            end
        end
endmodule

module MUX2_1(output reg [2:0] OUT, input [2:0] Io, input [2:0] I1, input S);
    always @(S or Io or I1)
        begin
            case(S)
                1'b0:    OUT = Io;
                1'b1:    OUT = I1;
                default: OUT = 3'dx;
            endcase
        end
endmodule

//8 to 1 MUX
module MUX8_1 (output reg [7:0] OUT, input [7:0] Io, input [7:0] I1, input [7:0] I2, input [7:0] I3, input [7:0] I4, input [7:0] I5, input [7:0] I6, input [7:0] I7, input [2:0] S);
    always @(S or Io or I1 or I2 or I3 or I4 or I5 or I6 or I7)
        begin
            case(S)
                3'b000:    OUT = Io;
                3'b001:    OUT = I1;
                3'b010:    OUT = I2;
                3'b011:    OUT = I3;
                3'b100:    OUT = I4;
                3'b101:    OUT = I5;
                3'b110:    OUT = I6;
                3'b111:    OUT = I7;
                default: OUT = 8'dx;
            endcase
        end
endmodule

module MUX4_1 (output reg [7:0] OUT, input [7:0] Io, input [7:0] I1, input [7:0] I2, input [7:0] I3, input [1:0] S); //4 to 1 MUX
    always @(S or Io or I1 or I2 or I3)
        begin
            case(S)
                2'd0: OUT = Io; //INPUT LOAD into OUT
                2'd1: OUT = I1; //MOVE Register(INSTR[2:0]) to Register(INSTR[5:3])
                2'd2: OUT = I2; //ADD Register(INSTR[2:0]) with A to store in Register(INSTR[5:3])
                2'd3: OUT = I3; //OUTPUT Register(INSTR[5:3])
                default: OUT = 8'dx;
            endcase
        end
endmodule

module DCDR3_8(output reg [7:0] OUT, input [2:0] IN); //3 to 8 Decoder
    always @(IN)
        begin
            case(IN)
                3'd0: OUT = 8'b00000001;
                3'd1: OUT = 8'b00000010;
                3'd2: OUT = 8'b00000100;
                3'd3: OUT = 8'b00001000;
                3'd4: OUT = 8'b00010000;
                3'd5: OUT = 8'b00100000;
                3'd6: OUT = 8'b01000000;
                3'd7: OUT = 8'b10000000;
                default: OUT = 8'd0;
            endcase
        end
endmodule

```

## Corresponding testbench Code

```
`timescale 1ns / 1ps
module Basic_Processor_struct_tb();
    reg CLK, RST;
    reg [7:0] ld_ext, instr;
    wire [7:0] OUT;
    Basic_Processor_Struct stimulus(instr, CLK, RST, ld_ext, OUT);
    initial begin
        CLK = 1'b0;
        RST = 1'b1;
//        forever #10 CLK = ~CLK; //time period of clock is 20 time units
    end
    initial begin
        #50
        begin
            RST = 1'b0;
            ld_ext = 8'd15; //load external value is 15
            instr = 8'b00000000; //Load value of 15 into A
            #10 CLK = ~CLK;
            #10 CLK = ~CLK;

        end

        #20 instr = 8'b11000111; //output value of A = 15 ----- 15
        #10 CLK = ~CLK;
        #10 CLK = ~CLK;

        #80 instr = 8'b01001000; //load value of A into B
        #10 CLK = ~CLK;
        #10 CLK = ~CLK;

        #60 instr = 8'b11001000; //output value of B = 15 --- 15
        #10 CLK = ~CLK;
        #10 CLK = ~CLK;

        #80 instr = 8'b10000001; //add value of A to B and store in A
        #10 CLK = ~CLK;
        #10 CLK = ~CLK;


        #40 instr = 8'b11000000; //output value of A -- ----- 15+15 = 30 -----30
        #10 CLK = ~CLK;
        #10 CLK = ~CLK;

        #80 instr = 8'b10000001; //add value of A to B and store in A
        #10 CLK = ~CLK;
        #10 CLK = ~CLK;

        #40 instr = 8'b11000000; //output value of A -- ----- 30+15 = 45 ----45
        #10 CLK = ~CLK;
        #10 CLK = ~CLK;

    end
    initial $monitor("Time: ", $time, " and Output = %d", OUT); //Printing the Output
    initial #(1000) $finish ;
endmodule
```

## Simulation

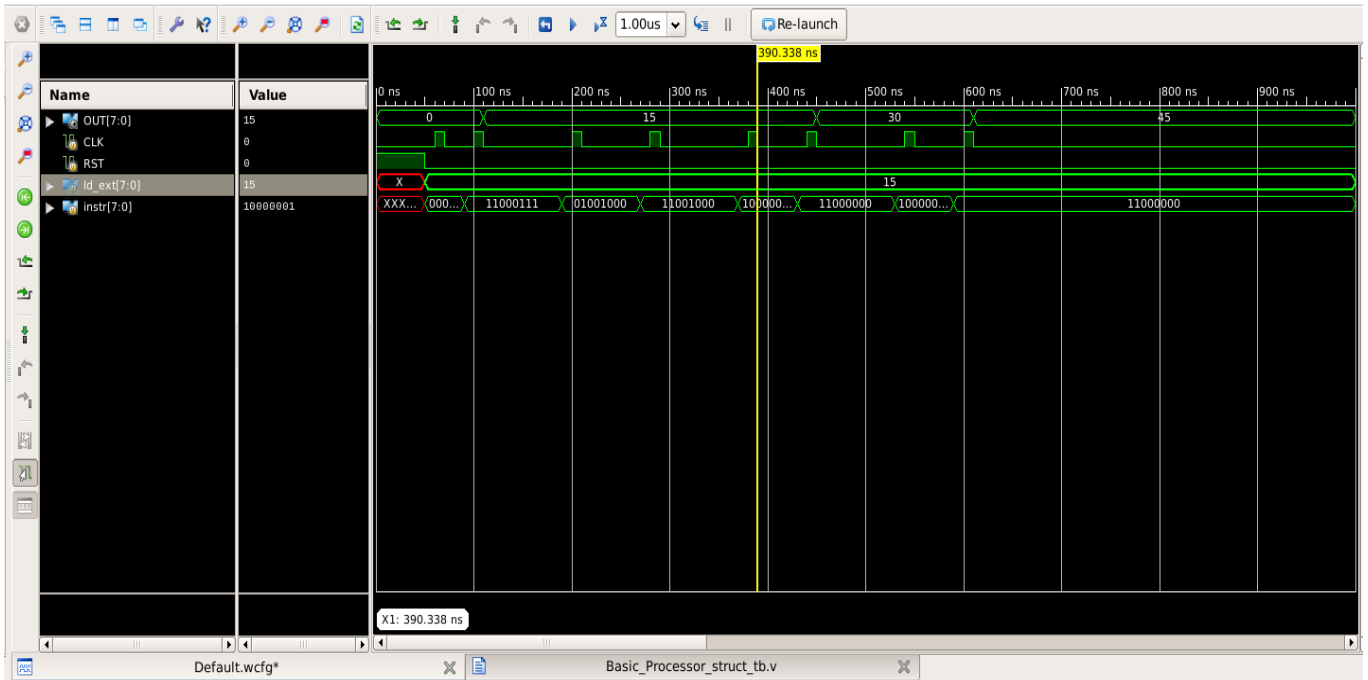

## Discussion:

- ✚ The sample case handled here is loading the value of A and making it thrice using the LD 15 -> IN A -> OUT A -> MOV B A -> OUT B -> ADD A B -> OUT A -> ADD A B -> OUT A. So, for given **input of 15**, **Output** value is **45**.
- ✚ Initially, all the values are RESET so as to reset any floating/unknown values.
- ✚ **After every instruction, only one period of clock** is given (nothing more nor less) so that any edge triggered components in the system complete only one operation. **If less**, they **wouldn't have moved to next state** and **if more**, they would have **moved forward by more than 1 state**. Hence, the **clock** in this experiment is **handled manually** unlike previous experiments.
- ✚ In the testbench, the inputs are registers type and outputs are wire type since the registers should go on supplying the same value until given another value (so **Input Port should have memory**) while the output keeps on changing according to any of the inputs (**Output Port has no memory**).
- ✚ In the simulated waveform, use the radix as unsigned decimal instead of binary (default) for easy viewing for decimal numbers.

## DRIVE LINK:

Structural File link is [here](#) (this file consists of only the Verilog code)

Corresponding Testbench is [here](#) (this file consists of only the testbench code)

*Both the files are separated to easily synthesize the RTL schematic and do any other analysis*